

### Design Methodology:

In this lab work we needed to show multiple digits of seven segment displays simultaneously. So, my aim is showing hexadecimal number on seven segment display with 16-bit binary number input with switches (when one of the switches is ON, the LED at the top of switch will be ON to distinguish which switches are ON.) Also I added push button input to reset clock counter signal and this feature gives us a chance to see which digit activated for a moment that we pressed push button.

When using seven segment displays, we can only send information for one digit at a time. So, to display multiple digits simultaneously we are using phenomenon called persistence of vision. In order to use this phenomenon, I wrote clock module that sends information to digits in loop with very high frequency. And I defined 4-2 multiplexer module in order to display every digits simultaneously with using my clock module. I defined switch of multiplexer as a clock counter signal (1downto0) and other inputs of multiplexer are switches with grouped by 4. (Such as 15downto12 is first digit, 11downto8 for second digit.) And as the outputs of multiplexer first output leads switch inputs to LED inputs such as "0001" and send the 4-bit output to our other module, decoder's input and second output directs the clock counter signals to activate anode. (Second output decides which digit will be displayed for a moment.) Also, showing letters and numbers in seven segment display is a bit complicated. Seven segment displays has seven LEDs with common anode and different cathodes. (there is one more LED for decimal point but I will ignore them for this lab work) We need to turn on appropriate LEDs to show our desirable digit. This situation does not have any math or logic. So we need to match our desired digits with 7-bit outputs. As I use 4-bit binary numbers to express every digit of 4-digit hexadecimal number, I defined decoder module to match 4-bit binary inputs from multiplexer module with 7-bit binary outputs. There are some figures that represent how seven segment displays work:

 


Figure 1: Seven Segment Displays' Common Anode LEDs

DIGITS	INPUTS				OUTPUTS						
					a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0
A	1	0	1	0	0	0	0	0	0	1	0
b	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
d	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	0	1	1	1	0	0	0

Figure 2: Truth Table for Decoder (4-bit binary to 7-segments matching)

After writing three modules and one top module, there is the RTL schematic of my design:

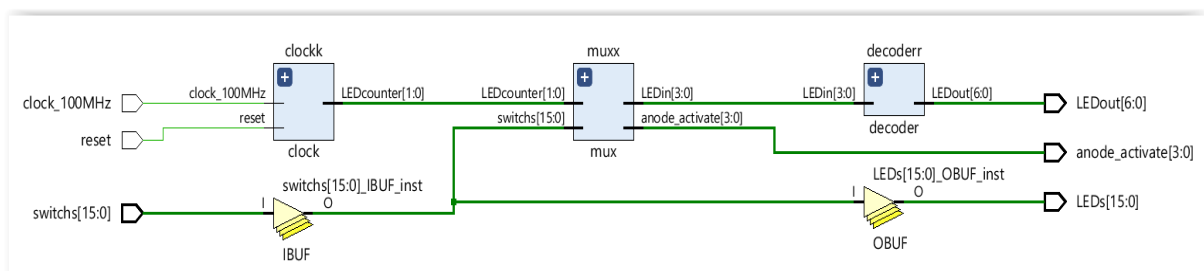


Figure 3: RTL Schematic of Design

## Results:

I wrote one top module, three modules and three test bench codes for each three module. After fixing some errors, it worked as what I expected.

There are schematics and behavioural simulations for each module:

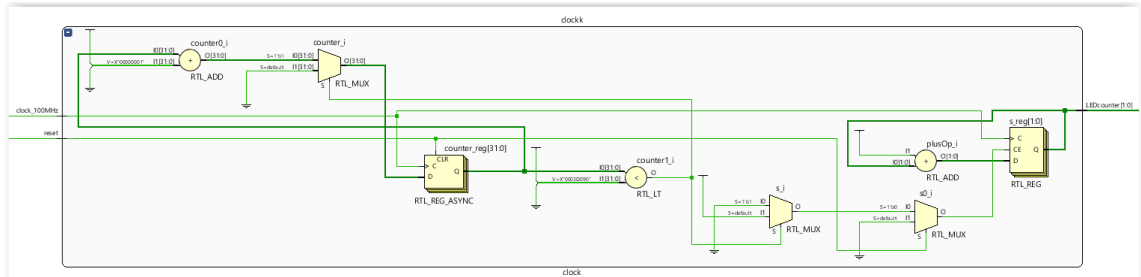


Figure 4: Schematic of Clock Module

 


Figure 5: Behavioural Simulation of Clock Module

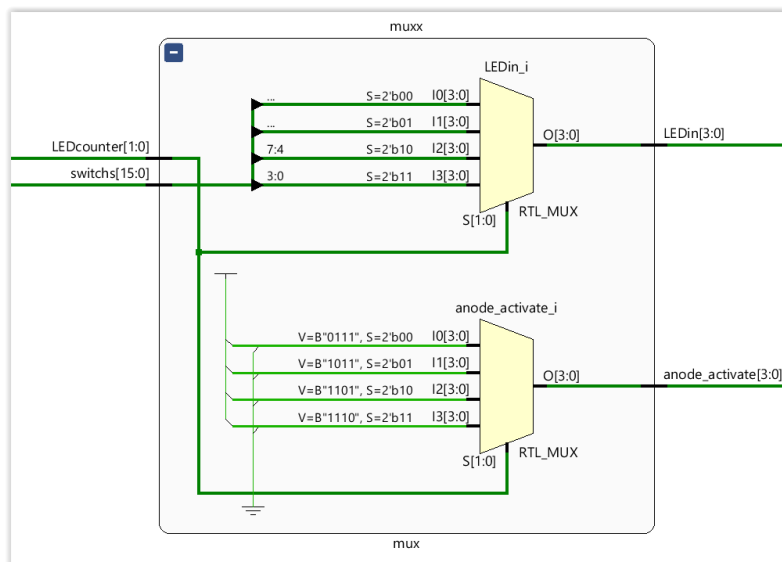


Figure 6: Schematic of Multiplexer Module

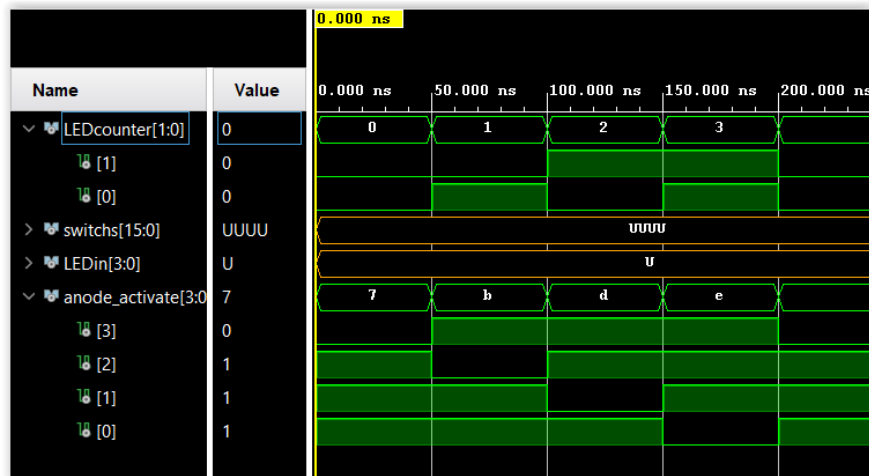


Figure 7: Behavioural Simulation of Multiplexer Module

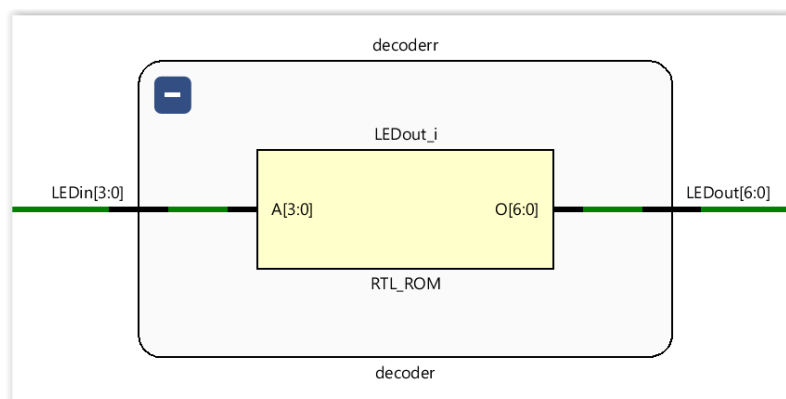


Figure 8: Schematic of Decoder Module

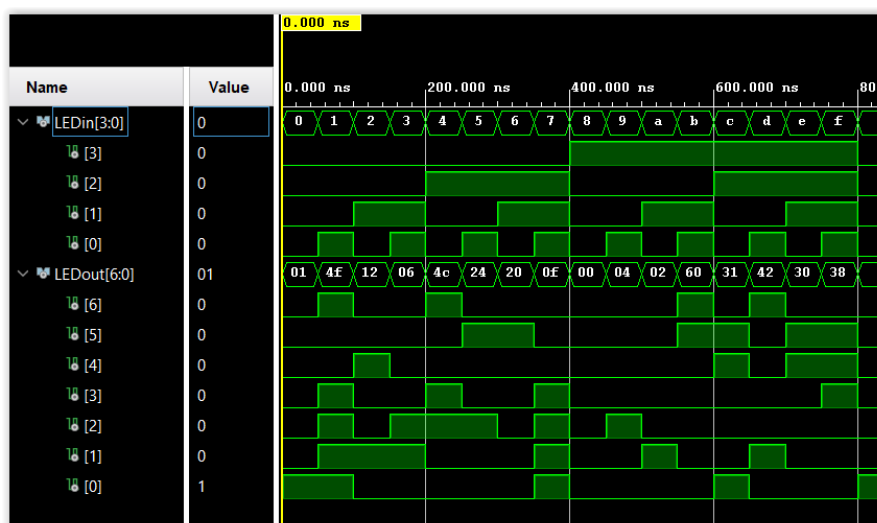


Figure 9: Behavioural Simulation of Decoder Module

Now, we generated bitstream to work our code on BASYS3. There are the test results:

 


Figure 10: Test 1 (0000-0000-0000-0000 => 0000)

 


Figure 11: Test 2 (0001-0010-0011-0100 => 1234)

 


Figure 12: Test 3 (0100-0011-0010-0001 => 4321)

Figure 15: Test 6 (1111-1111-1111-1111 => FFFF)



## Conclusion:

In this lab work, I learned how to code seven segment displays with VHDL. Seven segment displays is a very essential concept for electronics because it is used in many electronic devices in real life. Also I learned how to do modular design. It is very useful for long and complicated projects. If we use modules, our code will be simpler and we can check for errors later easier than non modular design. In order to do behavioural simulation in modular design, I learned that I need to write test bench for every module separately. In the test part on BASYS3, I confronted an error. My digits displays were inverse. (**E** → **3** , **7** → **1**) Then I realized that I wrote orders of seven segment displays constraints inversely (0->6 instead of 6->0) I corrected order of constraints and it worked as I expected.

## Appendices:

### Top Module:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity seven_segment is
```

```
Port (
```

```
    clock_100MHz: in std_logic;
```

```
    reset: in std_logic;
```

```
    switchs: in std_logic_vector (15 downto 0);
```

```
    LEDout: out std_logic_vector (6 downto 0);
```

```
    anode_activate: out std_logic_vector (3 downto 0);
```

```
    LEDs: out std_logic_vector (15 downto 0)
```

```
);
```

```
end seven_segment;
```

architecture Behavioral of seven\_segment is

component clock is

Port (

clock\_100MHz: in std\_logic;

reset: in std\_logic;

LEDcounter: out std\_logic\_vector (1 downto 0)

);

end component;

component decoder is -- decoder kullanarak 0001 ile 0000001'i eşleştiriyoruz

Port (

LEDin: in std\_logic\_vector (3 downto 0);

LEDout: out std\_logic\_vector (6 downto 0)

);

end component;

component mux is -- 4-1 multiplexer ile switchleri ledlere göre 4'lü grupluyoruz

Port (

LEDcounter: in std\_logic\_vector (1 downto 0);

switchs: in std\_logic\_vector (15 downto 0);

LEDin: out std\_logic\_vector (3 downto 0);

anode\_activate: out std\_logic\_vector (3 downto 0)

);



end component;

signal LEDcounter: std\_logic\_vector (1 downto 0);

signal LEDin: std\_logic\_vector (3 downto 0);

begin

LEDs <= switches;

clockk: clock port map ( clock\_100MHz => clock\_100MHz, reset => reset, LEDcounter => LEDcounter);

decoderr: decoder port map ( LEDin => LEDin, LEDout => LEDout);

muxx: mux port map ( LEDcounter => LEDcounter, switchs => switches, LEDin => LEDin, anode\_activate => anode\_activate);

end Behavioral;

#### **Clock Module:**

-----

-- Company:

-- Engineer:

--

-- Create Date: 20.03.2021 18:54:57

-- Design Name:

-- Module Name: clock - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

-----

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

use IEEE.std\_logic\_unsigned.all;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC\_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity clock is

```
Port (  
    clock_100MHz: in std_logic;  
    reset: in std_logic;  
    LEDcounter: out std_logic_vector (1 downto 0)  
);  
end clock;
```

architecture Behavioral of clock is

```
    signal counter: integer:= 0;  
    signal s : std_logic_vector (1 downto 0);  
begin  
    process(clock_100MHz)  
    begin  
        if reset='1' then  
            counter <= 0;  
        elsif rising_edge(clock_100MHz) then  
            if counter < 250000 then  
                counter <= counter + 1;  
            else  
                counter <= 0;  
                s <= s+1;  
            end if;  
        end if;  
    end process;
```

```
        end if;

    end process;

    LEDcounter <= std_logic_vector(s);

end Behavioral;
```

### **Multiplexer Module:**

```
-----

-- Company:
-- Engineer:
--
-- Create Date: 20.03.2021 18:41:34
-- Design Name:
-- Module Name: mux - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
```

-- Additional Comments:

--

-----

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC\_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity mux is

Port (

LEDcounter: in std\_logic\_vector (1 downto 0);

switchs: in std\_logic\_vector (15 downto 0);

LEDin: out std\_logic\_vector (3 downto 0);

anode\_activate: out std\_logic\_vector (3 downto 0)

);

end mux;

architecture Behavioral of mux is

begin

process(LEDcounter)

begin

case LEDcounter is

when "00" =>

anode\_activate <= "0111"; --LED1 is activated

LEDin <= switchs(15 downto 12);

when "01" =>

anode\_activate <= "1011"; --LED2 is activated

LEDin <= switchs(11 downto 8);

when "10" =>

anode\_activate <= "1101"; --LED3 is activated

LEDin <= switchs(7 downto 4);

when "11" =>

anode\_activate <= "1110"; --LED2 is activated

LEDin <= switchs(3 downto 0);

when others =>

anode\_activate <= "1111"; --no LED activated

LEDin <= "0000";

end case;

end process;

end Behavioral;

**Decoder Module:**

-----

-- Company:

-- Engineer:

--

-- Create Date: 20.03.2021 17:49:24

-- Design Name:

-- Module Name: decoder - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--



-----

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity decoder is
    Port (
        LEDin: in std_logic_vector (3 downto 0);
        LEDout: out std_logic_vector (6 downto 0)
    );
end decoder;

architecture Behavioral of decoder is
```

```
begin

  process(LEDin)

    begin

      case LEDin is

        when "0000" => LEDout <= "0000001"; --0

        when "0001" => LEDout <= "1001111"; --1

        when "0010" => LEDout <= "0010010"; --2

        when "0011" => LEDout <= "0000110"; --3

        when "0100" => LEDout <= "1001100"; --4

        when "0101" => LEDout <= "0100100"; --5

        when "0110" => LEDout <= "0100000"; --6

        when "0111" => LEDout <= "0001111"; --7

        when "1000" => LEDout <= "0000000"; --8

        when "1001" => LEDout <= "0000100"; --9

        when "1010" => LEDout <= "0000010"; --a

        when "1011" => LEDout <= "1100000"; --b

        when "1100" => LEDout <= "0110001"; --C

        when "1101" => LEDout <= "1000010"; --d

        when "1110" => LEDout <= "0110000"; --E

        when "1111" => LEDout <= "0111000"; --F

        when others => LEDout <= "1111111"; --no LED activated

      end case;

    end process;
```

end Behavioral;

**Test Bench for Clock Module:**

-----

-- Company:

-- Engineer:

--

-- Create Date: 26.03.2021 13:58:41

-- Design Name:

-- Module Name: tb\_clock - Behavioral

-- Project Name:

-- Target Devices:

-- Tool Versions:

-- Description:

--

-- Dependencies:

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

-----

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity tb_clock is end;


architecture Behavioral of tb_clock is

component clock

Port(

    clock_100MHz: in std_logic;

    reset: in std_logic;

    LEDcounter: out std_logic_vector(1 downto 0)

);

end component;
```

```
signal clock_100MHz: std_logic;  
  
signal reset: std_logic;  
  
signal LEDcounter: std_logic_vector(1 downto 0);
```

```
constant clock_period: time:=50ns;  
  
signal clock_stop: boolean;
```

```
begin
```

```
portmap: clock port map(  
    clock_100MHz => clock_100MHz,  
    reset => reset,  
    LEDcounter => LEDcounter  
);
```

```
process
```

```
begin
```

```
    while not clock_stop
```

```
    loop
```

```
        clock_100MHz <= '0','1'
```

```
        after clock_period/2;
```

```
        wait for clock_period;
```

```
    end loop;
```

```
    wait;
```

```
end process;  
  
end Behavioral;
```

#### **Test Bench for Multiplexer Module:**

```
-----  
  
-- Company:  
  
-- Engineer:  
  
--  
  
-- Create Date: 26.03.2021 14:19:49  
  
-- Design Name:  
  
-- Module Name: tb_mux - Behavioral  
  
-- Project Name:  
  
-- Target Devices:  
  
-- Tool Versions:  
  
-- Description:  
  
--  
  
-- Dependencies:  
  
--  
  
-- Revision:  
  
-- Revision 0.01 - File Created  
  
-- Additional Comments:  
  
--  
  
-----
```

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;


-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity tb_mux is end;


architecture Behavioral of tb_mux is
    component mux

        Port (
            LEDcounter: in std_logic_vector (1 downto 0);
            switchs: in std_logic_vector (15 downto 0);
            LEDin: out std_logic_vector (3 downto 0);
```



```
        anode_activate: out std_logic_vector (3 downto 0)
    );
end component;
```

```
signal LEDcounter: std_logic_vector (1 downto 0);
signal switchs: std_logic_vector (15 downto 0);
signal LEDin: std_logic_vector (3 downto 0);
signal anode_activate: std_logic_vector (3 downto 0);
```

```
begin
```

```
    portmap: mux port map
    (
        LEDcounter => LEDcounter,
        switchs => switchs,
        LEDin => LEDin,
        anode_activate => anode_activate
    );
```

```
process
begin
    LEDcounter <= "00";

    wait for 50ns;

    LEDcounter <= "01";
```

```
wait for 50ns;  
  
LEDcounter <= "10";  
  
wait for 50ns;  
  
LEDcounter <= "11";  
  
wait for 50ns;  
  
wait;  
  
end process;
```

```
end Behavioral;
```

#### **Test Bench for Decoder Module:**

-----

```
-- Company:  
  
-- Engineer:  
  
--  
  
-- Create Date: 26.03.2021 15:06:22  
  
-- Design Name:  
  
-- Module Name: tb_decoder - Behavioral  
  
-- Project Name:  
  
-- Target Devices:  
  
-- Tool Versions:  
  
-- Description:  
  
--  
  
-- Dependencies:
```

--

-- Revision:

-- Revision 0.01 - File Created

-- Additional Comments:

--

-----

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

-- Uncomment the following library declaration if using

-- arithmetic functions with Signed or Unsigned values

--use IEEE.NUMERIC\_STD.ALL;

-- Uncomment the following library declaration if instantiating

-- any Xilinx leaf cells in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity tb\_decoder is end;

architecture Behavioral of tb\_decoder is

component decoder

```
Port (  
    LEDin: in std_logic_vector (3 downto 0);  
    LEDout: out std_logic_vector (6 downto 0)  
);  
end component;
```

```
signal LEDin: std_logic_vector (3 downto 0);  
signal LEDout: std_logic_vector (6 downto 0);
```

```
begin
```

```
portmap: decoder port map
```

```
(  
    LEDin => LEDin,  
    LEDout => LEDout  
);
```

```
process
```

```
begin
```

```
LEDin <= "0000";
```

```
wait for 50ns;
```

```
LEDin <= "0001";
```

```
wait for 50ns;
```

LEDin <= "0010";

wait for 50ns;

LEDin <= "0011";

wait for 50ns;

LEDin <= "0100";

wait for 50ns;

LEDin <= "0101";

wait for 50ns;

LEDin <= "0110";

wait for 50ns;

LEDin <= "0111";

wait for 50ns;

LEDin <= "1000";

wait for 50ns;

LEDin <= "1001";

wait for 50ns;

LEDin <= "1010";

wait for 50ns;

LEDin <= "1011";

wait for 50ns;

LEDin <= "1100";

wait for 50ns;

LEDin <= "1101";

wait for 50ns;

```
LEDin <= "1110";  
  
wait for 50ns;  
  
LEDin <= "1111";  
  
wait for 50ns;  
  
LEDin <= "0000";  
  
wait;  
  
end process;  
  
end Behavioral;
```

#### **Constraints :**

# Clock signal

```
set_property PACKAGE_PIN W5 [get_ports clock_100MHz]  
  
    set_property IOSTANDARD LVCMOS33 [get_ports clock_100MHz]  
  
set_property PACKAGE_PIN U18 [get_ports reset]  
  
    set_property IOSTANDARD LVCMOS33 [get_ports reset]
```

# Switches

```
set_property PACKAGE_PIN V17 [get_ports {switchs[0]}]  
  
    set_property IOSTANDARD LVCMOS33 [get_ports {switchs[0]}]  
  
set_property PACKAGE_PIN V16 [get_ports {switchs[1]}]  
  
    set_property IOSTANDARD LVCMOS33 [get_ports {switchs[1]}]  
  
set_property PACKAGE_PIN W16 [get_ports {switchs[2]}]  
  
    set_property IOSTANDARD LVCMOS33 [get_ports {switchs[2]}]  
  
set_property PACKAGE_PIN W17 [get_ports {switchs[3]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[3]]}
set_property PACKAGE_PIN W15 [get_ports {switchs[4]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[4]]}
set_property PACKAGE_PIN V15 [get_ports {switchs[5]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[5]]}
set_property PACKAGE_PIN W14 [get_ports {switchs[6]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[6]]}
set_property PACKAGE_PIN W13 [get_ports {switchs[7]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[7]]}
set_property PACKAGE_PIN V2 [get_ports {switchs[8]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[8]]}
set_property PACKAGE_PIN T3 [get_ports {switchs[9]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[9]]}
set_property PACKAGE_PIN T2 [get_ports {switchs[10]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[10]]}
set_property PACKAGE_PIN R3 [get_ports {switchs[11]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[11]]}
set_property PACKAGE_PIN W2 [get_ports {switchs[12]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[12]]}
set_property PACKAGE_PIN U1 [get_ports {switchs[13]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[13]]}
set_property PACKAGE_PIN T1 [get_ports {switchs[14]]}
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[14]]}
set_property PACKAGE_PIN R2 [get_ports {switchs[15]]}
```



```
set_property IOSTANDARD LVCMOS33 [get_ports {switchs[15]]}

set_property IOSTANDARD LVCMOS33 [get_ports {switchs[15]]}


# LEDs

set_property PACKAGE_PIN U16 [get_ports {LEDs[0]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[0]]}

set_property PACKAGE_PIN E19 [get_ports {LEDs[1]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[1]]}

set_property PACKAGE_PIN U19 [get_ports {LEDs[2]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[2]]}

set_property PACKAGE_PIN V19 [get_ports {LEDs[3]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[3]]}

set_property PACKAGE_PIN W18 [get_ports {LEDs[4]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[4]]}

set_property PACKAGE_PIN U15 [get_ports {LEDs[5]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[5]]}

set_property PACKAGE_PIN U14 [get_ports {LEDs[6]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[6]]}

set_property PACKAGE_PIN V14 [get_ports {LEDs[7]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[7]]}

set_property PACKAGE_PIN V13 [get_ports {LEDs[8]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[8]]}

set_property PACKAGE_PIN V3 [get_ports {LEDs[9]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[9]]}
```

```
set_property PACKAGE_PIN W3 [get_ports {LEDs[10]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[10]]}

set_property PACKAGE_PIN U3 [get_ports {LEDs[11]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[11]]}

set_property PACKAGE_PIN P3 [get_ports {LEDs[12]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[12]]}

set_property PACKAGE_PIN N3 [get_ports {LEDs[13]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[13]]}

set_property PACKAGE_PIN P1 [get_ports {LEDs[14]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[14]]}

set_property PACKAGE_PIN L1 [get_ports {LEDs[15]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[15]]}
```

#7 segment display

```
set_property PACKAGE_PIN W7 [get_ports {LEDout[6]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[6]]}

set_property PACKAGE_PIN W6 [get_ports {LEDout[5]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[5]]}

set_property PACKAGE_PIN U8 [get_ports {LEDout[4]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[4]]}

set_property PACKAGE_PIN V8 [get_ports {LEDout[3]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[3]]}

set_property PACKAGE_PIN U5 [get_ports {LEDout[2]]}

    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[2]]}
```

```
set_property PACKAGE_PIN V5 [get_ports {LEDout[1]]}

set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[1]]}

set_property PACKAGE_PIN U7 [get_ports {LEDout[0]]}

set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[0]]}

set_property PACKAGE_PIN U2 [get_ports {anode_activate[0]]}

set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[0]]}

set_property PACKAGE_PIN U4 [get_ports {anode_activate[1]]}

set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[1]]}

set_property PACKAGE_PIN V4 [get_ports {anode_activate[2]]}

set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[2]]}

set_property PACKAGE_PIN W4 [get_ports {anode_activate[3]]}

set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[3]]}
```