

Design Methodology:

In this lab work, we needed to design circuit with ALU. After some research, I realized that usage of Arithmetic-Logic Unit in VHDL is very easy. If I use unsigned and numeric libraries, I can do any kind of Arithmetic-Logic operation in PROCESS and IF with only using signs such as +, AND, > etc. We needed to do at least 8 operations and so I did these operations:

000 – ADDITION	001 – SUBTRACTION
010 – ADD WITH CARRY	011 – COMPARISON
100 – AND	101 – SHIFT LEFT
110 – SHIFT RIGHT	111 – ROTATE RIGHT

Table 1: Operations

In order to show my design's outputs, I decided to use seven segment displays. In the previous lab, we learned to use seven segment displays and I used these codes with some enhancement in this lab work. As seen below, I used 3-bit binary numbers as inputs (A and B) and I defined these inputs with 3 switches each. Also I needed to "Select" input and I defined this 3-bit binary input with 3 switches. As output, I used seven segment displays' last three digits to show 3-bit binary output for all operations except "add with carry". In the "add with carry" operation, I used 4-bit binary as output and used all 4 digits of seven segment displays. Therefore, I have an "error LED" which shows us there is a problem about operation. I used "error LED" in only two operations that are "addition" and "subtraction". In the addition op., error LED shows there is a carry out digit which we cannot show in 3-bit binary output; in the subtraction op., error LED shows there is needed carry in.

 


Figure 1: Locations of inputs and outputs

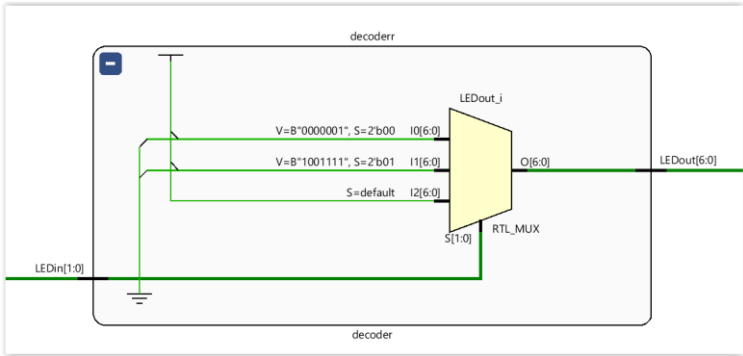


Figure 5: Schematic of Decoder Module

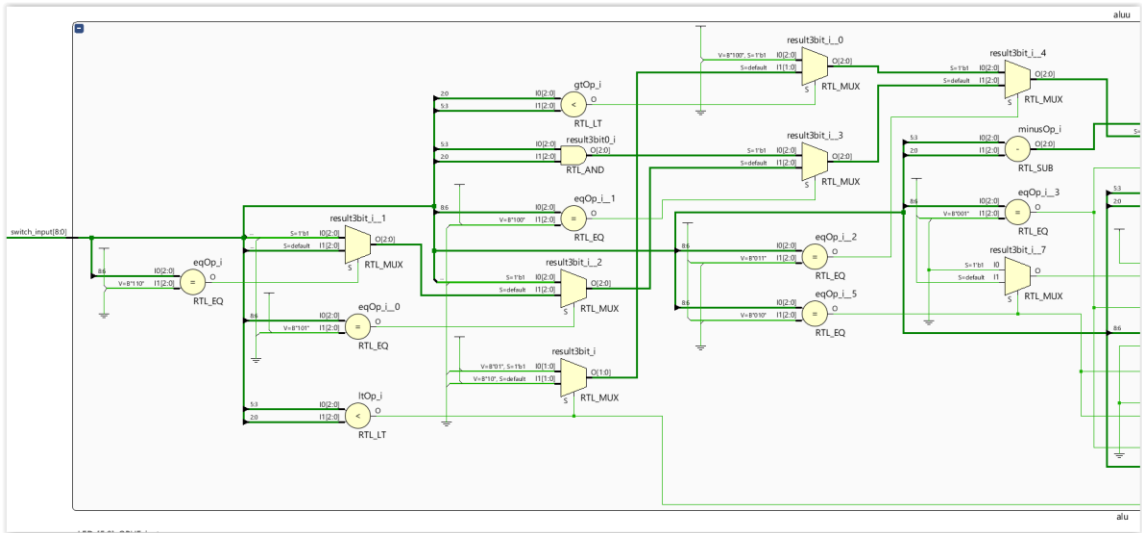


Figure 6: Schematic of First Part of Alu Module

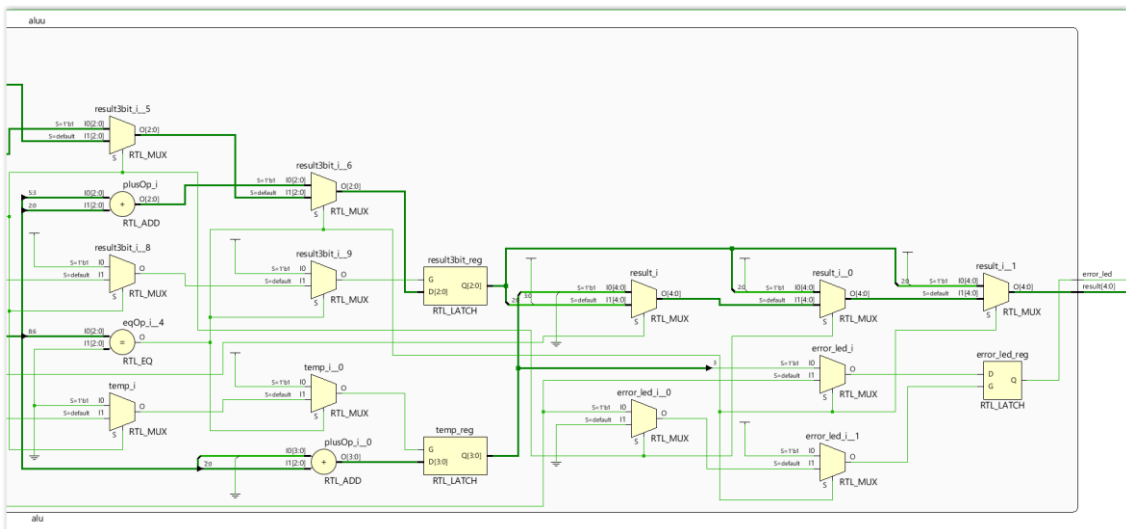


Figure 7: Schematic of Second Part of Alu Module

 


Figure 8: Demo 1 => Addition (000) => 011 + 011 = 110

 


Figure 9: Demo 2 => Addition (000) => 111 + 111 = 110 (Error LED)

 


Figure 10: Demo 3 => Subtraction (001) => $111 - 010 = 101$

 


Figure 11: Demo 4 => Subtraction (001) => $000 - 001 = 111$ (Error LED)

 


Figure 12: Demo 5 => Add with Carry (010) => $111 + 111 = 1110$

 


Figure 13: Demo 6 => Comparison (011) => $001 = 001$ (Equal means 010 in displays)

 


Figure 14: Demo 7 => Comparison (011) => 011 > 001 (A > B means 001)

 


Figure 15: Demo 8 => Comparison (011) => 001 < 011 (A < B means 100)

 


Figure 16: Demo 9 => AND (100) => 111 AND 101 = 101

 


Figure 17: Demo 10 => Shift Left (101) => Shift Left (111) = 110

 


Figure 18: Demo 11 => Shift Right (110) => Shift Right(111) = 011

 


Figure 19: Demo 12 => Rotate Right (111) => Rotate Right(110) = 011

Conclusion:

In this lab work, I learned to do arithmetic and logical operations in VHDL. It was easy due to unsigned and numeric libraries. With only usage of mathematical signs of operations, I could reach my intended result. When I writing addition operation, carry out was the problem. But I defined this operation as:

```
result3bit <= switch_input(5 downto 3) + switch_input(2 downto 0); -- add  
temp <= ('0' & switch_input(5 downto 3)) + switch_input(2 downto 0);  
error_led <= temp(3);  
result <= "11" & result3bit;
```

and I could able to show my 3 digit result and light error LED if there is carry out digit.

Also, I concatenated some two digit vector (LEDin) with result3bit and I tried to open first digit of seven segment display only when we select “add with carry” operation. For other cases, I wanted to hide first digit. For this case, in the decoder module, I used this two digit vector as:

```
case LEDin is  
    when "00" => LEDout <= "0000001"; --0  
    when "01" => LEDout <= "1001111"; --1  
    when others => LEDout <= "1111111"; --no LED activated  
end case;
```

and I achieved to hide first digit when operation is not “add with carry”. I did this with concatenated ‘0’ at the beginning of each last three digits’ outputs in the multiplexer, such as:

```
case LEDcounter is  
    when "00" =>  
        anode_activate <= "0111"; --LED1 is activated  
        LEDin <= result(4 downto 3);  
    when "01" =>  
        anode_activate <= "1011"; --LED2 is activated  
        LEDin <= '0' & result(2);
```


So, if LEDin(for first digit of seven segment displays) is “11” or “10”, first LED will not be activated. For all operations except “add with carry”, I used this line of code:

```
result <= "11" & result3bit;
```

In the add with carry operation, I used this lines of code:

```
temp <= ('0' & switch_input(5 downto 3)) + switch_input(2 downto 0); --add with carry  
result <= '0' & temp;
```

So, the output of “add with carry” operation will be 4-bit binary and first digit of seven segment displays will work for this operation. Because LEDin for first(for first digit of seven segment displays) will be “01” or “00” for this operation.

Appendices:

Top Module:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use IEEE.std_logic_unsigned.all;

entity main_lab5 is

Port(

switch_input: in std_logic_vector(8 downto 0);

clock_100MHz: in std_logic;

LEDout: out std_logic_vector (6 downto 0);

anode_activate: out std_logic_vector (3 downto 0);

LEDs: out std_logic_vector (9 downto 0)

);

end main_lab5;

architecture Behavioral of main_lab5 is

component clock is

```
Port (  
    clock_100MHz: in std_logic;  
    LEDcounter: out std_logic_vector (1 downto 0)  
);  
end component;
```

component mux is -- 4-1 multiplexer ile switchleri ledlere göre 4'lü grupluyoruz

```
Port (  
    LEDcounter: in std_logic_vector (1 downto 0);  
    switch_input: in std_logic_vector (8 downto 0);  
    LEDin: out std_logic_vector (1 downto 0);  
    anode_activate: out std_logic_vector (3 downto 0);  
    result: in std_logic_vector (4 downto 0)  
);  
end component;
```

component decoder is -- decoder kullanarak 0001 ile 0000001'i eşleştiriyoruz

```
Port (  
    LEDin: in std_logic_vector(1 downto 0);  
    LEDout: out std_logic_vector (6 downto 0)  
);  
end component;
```

component alu is -- decoder kullanarak 0001 ile 0000001'i eşleştiriyoruz

Port (

switch_input: in std_logic_vector(8 downto 0);

result: out std_logic_vector (4 downto 0);

error_led: out std_logic

);

end component;

signal LEDcounter: std_logic_vector (1 downto 0);

signal LEDin: std_logic_vector (1 downto 0);

signal result: std_logic_vector (4 downto 0);

signal error_led: std_logic;

begin

LEDs(9 downto 7) <= switch_input(8 downto 6);

LEDs(5 downto 3) <= switch_input(5 downto 3);

LEDs(2 downto 0) <= switch_input(2 downto 0);

LEDS(6) <= error_led;

clockk: clock port map (clock_100MHz => clock_100MHz, LEDcounter => LEDcounter);

decoderr: decoder port map (LEDin => LEDin, LEDout => LEDout);

muxx: mux port map (LEDcounter => LEDcounter, switch_input => switch_input, LEDin => LEDin,
anode_activate => anode_activate, result => result);

aluu: alu port map (switch_input => switch_input, result => result, error_led => error_led);

end Behavioral;

ALU module:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity alu is
```

```
    Port(
```

```
        switch_input: in std_logic_vector(8 downto 0);
```

```
        result: out std_logic_vector (4 downto 0);
```

```
        error_led: out std_logic
```

```
    );
```

```
end alu;
```

```
architecture Behavioral of alu is
```

```
    signal temp: std_logic_vector (3 downto 0);
```

```
    signal result3bit: std_logic_vector (2 downto 0);
```

```
begin
```

```
    process(switch_input)
```

```
    begin
```

```
        if switch_input(8 downto 6) = "000" then
```

```
            result3bit <= switch_input(5 downto 3) + switch_input(2 downto 0); -- add
```

```
            temp <= ('0' & switch_input(5 downto 3)) + switch_input(2 downto 0);
```

```
            error_led <= temp(3);
```

```
            result <= "11" & result3bit;
```



```
elseif switch_input(8 downto 6) = "001" then

    result3bit <= switch_input(5 downto 3) - switch_input(2 downto 0); --subtract

    result <= "11" & result3bit;

    if switch_input(5 downto 3) < switch_input(2 downto 0) then

        error_led <= '1';

    end if;

elseif switch_input(8 downto 6) = "010" then

    temp <= ('0' & switch_input(5 downto 3)) + switch_input(2 downto 0); --add with carry

    result <= '0' & temp;

elseif switch_input(8 downto 6) = "011" then

    if switch_input(5 downto 3) > switch_input(2 downto 0) then --comparison

        result3bit <= "100";

        result <= "11" & result3bit;

    elseif switch_input(5 downto 3) < switch_input(2 downto 0) then

        result3bit <= "001";

        result <= "11" & result3bit;

    else

        result3bit <= "010";

        result <= "11" & result3bit;

    end if;

elseif switch_input(8 downto 6) = "100" then

    result3bit <= switch_input(5 downto 3) AND switch_input(2 downto 0); --AND

    result <= "11" & result3bit;

elseif switch_input(8 downto 6) = "101" then

    result3bit <= switch_input(1 downto 0) & '0'; --shift left

    result <= "11" & result3bit;
```

```
elseif switch_input(8 downto 6) = "110" then
    result3bit <= '0' & switch_input(2 downto 1) ; --shift right
    result <= "11" & result3bit;
else
    result3bit <= switch_input(0) & switch_input(2 downto 1); --rotate right
    result <= "11" & result3bit;
end if;
end process;
end Behavioral;
```

Clock module:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity clock is
    Port (
        clock_100MHz: in std_logic;
        LEDcounter: out std_logic_vector (1 downto 0)
    );
end clock;
```

architecture Behavioral of clock is

```
    signal counter: integer:= 0;
    signal s : std_logic_vector (1 downto 0);
begin
```

```
process(clock_100MHz)
begin
    if rising_edge(clock_100MHz) then
        if counter < 250000 then
            counter <= counter + 1;
        else
            counter <= 0;
            s <= s+1;
        end if;
    end if;
end process;
```

```
LEDcounter <= std_logic_vector(s);
end Behavioral;
```

Multiplexer Module:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.std_logic_unsigned.all;
entity mux is
    Port (
        LEDcounter: in std_logic_vector (1 downto 0);
        switch_input: in std_logic_vector (8 downto 0);
        LEDin: out std_logic_vector(1 downto 0);
        anode_activate: out std_logic_vector (3 downto 0);
```

```
    result: in std_logic_vector (4 downto 0)

);

end mux;
```

architecture Behavioral of mux is

```
begin
```

```
    process(LEDcounter)
```

```
    begin
```

```
        case LEDcounter is
```

```
            when "00" =>
```

```
                anode_activate <= "0111"; --LED1 is activated
```

```
                LEDin <= result(4 downto 3);
```

```
            when "01" =>
```

```
                anode_activate <= "1011"; --LED2 is activated
```

```
                LEDin <= '0' & result(2);
```

```
            when "10" =>
```

```
                anode_activate <= "1101"; --LED3 is activated
```

```
                LEDin <= '0' & result(1);
```

```
            when others =>
```

```
                anode_activate <= "1110"; --LED2 is activated
```

```
                LEDin <= '0' & result(0);
```

```
        end case;
```

```
    end process;
```

```
end Behavioral;
```


Decoder Module:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity decoder is

```
Port (
```

```
    LEDin: in std_logic_vector(1 downto 0);
```

```
    LEDout: out std_logic_vector (6 downto 0)
```

```
);
```

```
end decoder;
```

architecture Behavioral of decoder is

```
begin
```

```
    process(LEDin)
```

```
    begin
```

```
        case LEDin is
```

```
            when "00" => LEDout <= "0000001"; --0
```

```
            when "01" => LEDout <= "1001111"; --1
```

```
            when others => LEDout <= "1111111"; --no LED activated
```

```
        end case;
```

```
    end process;
```

```
end Behavioral;
```

Constraints:

Clock signal

```
set_property PACKAGE_PIN W5 [get_ports clock_100MHz]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports clock_100MHz]
```

Switches

```
set_property PACKAGE_PIN V17 [get_ports {switch_input[0]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[0]}]
```

```
set_property PACKAGE_PIN V16 [get_ports {switch_input[1]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[1]}]
```

```
set_property PACKAGE_PIN W16 [get_ports {switch_input[2]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[2]}]
```

```
set_property PACKAGE_PIN W17 [get_ports {switch_input[3]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[3]}]
```

```
set_property PACKAGE_PIN W15 [get_ports {switch_input[4]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[4]}]
```

```
set_property PACKAGE_PIN V15 [get_ports {switch_input[5]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[5]}]
```

```
set_property PACKAGE_PIN U1 [get_ports {switch_input[6]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[6]}]
```

```
set_property PACKAGE_PIN T1 [get_ports {switch_input[7]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[7]}]
```

```
set_property PACKAGE_PIN R2 [get_ports {switch_input[8]}]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports {switch_input[8]}]
```

LEDs

```
set_property PACKAGE_PIN U16 [get_ports {LEDs[0]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[0]]  
set_property PACKAGE_PIN E19 [get_ports {LEDs[1]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[1]]  
set_property PACKAGE_PIN U19 [get_ports {LEDs[2]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[2]]  
set_property PACKAGE_PIN V19 [get_ports {LEDs[3]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[3]]  
set_property PACKAGE_PIN W18 [get_ports {LEDs[4]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[4]]  
set_property PACKAGE_PIN U15 [get_ports {LEDs[5]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[5]]  
  
set_property PACKAGE_PIN V13 [get_ports {LEDs[6]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[6]]  
  
set_property PACKAGE_PIN N3 [get_ports {LEDs[7]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[7]]  
set_property PACKAGE_PIN P1 [get_ports {LEDs[8]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[8]]  
set_property PACKAGE_PIN L1 [get_ports {LEDs[9]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[9]]
```

#7 segment display

```
set_property PACKAGE_PIN W7 [get_ports {LEDout[6]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[6]]
set_property PACKAGE_PIN W6 [get_ports {LEDout[5]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[5]]
set_property PACKAGE_PIN U8 [get_ports {LEDout[4]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[4]]
set_property PACKAGE_PIN V8 [get_ports {LEDout[3]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[3]]
set_property PACKAGE_PIN U5 [get_ports {LEDout[2]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[2]]
set_property PACKAGE_PIN V5 [get_ports {LEDout[1]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[1]]
set_property PACKAGE_PIN U7 [get_ports {LEDout[0]]
    set_property IOSTANDARD LVCMOS33 [get_ports {LEDout[0]]

set_property PACKAGE_PIN U2 [get_ports {anode_activate[0]]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[0]]
set_property PACKAGE_PIN U4 [get_ports {anode_activate[1]]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[1]]
set_property PACKAGE_PIN V4 [get_ports {anode_activate[2]]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[2]]
set_property PACKAGE_PIN W4 [get_ports {anode_activate[3]]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode_activate[3]]
```